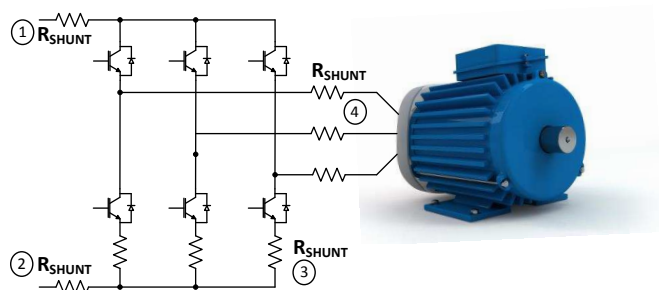


# Low-Drift, Low-Side Current Measurements for Three-Phase Systems

Scott Hill, Current Sensing Products



There are multiple locations in the drive circuitry for a motor where the motor's **phase currents** can be measured. How the current information will be used by the system controller plays a large role in determining the measurement location that **aligns best**. The four most common locations to measure current in a three-phase motor are shown in **Figure 1**. There are trade-offs associated with each of the measurement locations such as the measurement accuracy capability, high-voltage circuitry requirements, and signal response time. The complexity of the measurement circuitry to provide adequate system control varies for each location.



**Figure 1. Measurement Locations In A Three-Phase System**

Measurement locations one and two from **Figure 1** are useful when the detection of faults is necessary rather than needing to provide information on the actual motor current back to the system controller. Extracting individual phase current information from these locations is challenging making them more ideal for comparisons of the total system currents to detect ground shorts, leakages, or other out-of-range conditions.

A common location to implement current sensing for motor control in three-phase systems is in the low-side of each phase leg (measurement location 3 from **Figure 1**) due to the **limited requirement on the common-mode voltage level**. In a low-side configuration it is important to note that **current only flows through each phase leg when that phase's low-side transistor is turned on**. The pulsed characteristic of the current in the low-side phase measurements is unlike the **continuous current at the in-line location** (measurement location 4 from **Figure 1**). Measuring the differential signal across a current sensing resistor

at location 4 allows for a continuous signal directly proportional to the motor's phase current. However, with the PWM motor drive circuitry creating large common-mode voltage level changes at this in-line location, specific current sense amplifiers capable of handling and rejecting these high dv/dt transitions are required.

In the low-side phase leg configuration the current flows through the shunt resistor only when that particular low-side transistor is on requiring **the amplifier to change output levels quickly as the current is pulsed off and on**. When this transistor turns on and begins to conduct current, the result is a stepped input signal. The amplifier must be able to respond quickly in amplifying the signal to allow the output to follow the input signal. A processor can then take the switched output waveform from the amplifier and re-combine the phase current information to extract the current signal that will be used in the motor's control algorithm.

A critical requirement for the current sense amplifier measuring low-side phase leg current is to be sufficiently fast to accommodate the small measurement time window determined by the PWM drive circuitry's switching frequency and duty cycle. The amplifier output must transition and settle before the measurement is sampled to provide an accurate proportional waveform to the actual phase current for the processor to use in the control algorithm.

The **bandwidth**, output drive and settling requirements are determined by the application's switching frequency and duty cycle range. **PWM switching frequencies in the range of 20kHz to 30kHz are common** in order to stay above the audible frequency band. For example, a 25kHz switching frequency with a 50% duty cycle and a sampling point taken at the midpoint of each half cycle requires the output of the current sense amplifier to settle within 10μs to ensure an accurate measurement. The processor is unable to create proportional waveforms for the control algorithms to properly control the motor if the amplifier's output is unable to reach the output level and sufficiently settle within the available time period.

The settling time period will change and vary as the duty cycle needed to control the motor is varied as shown in **Figure 2**. Lower motor speeds require a lower duty cycle creating a challenge for the current sense amplifier to provide accurate measurements

with smaller timing periods. The duty cycle required to provide the necessary control capability in the motor's control algorithm will determine the necessary bandwidth and settling time characteristics of the current sense amplifier.

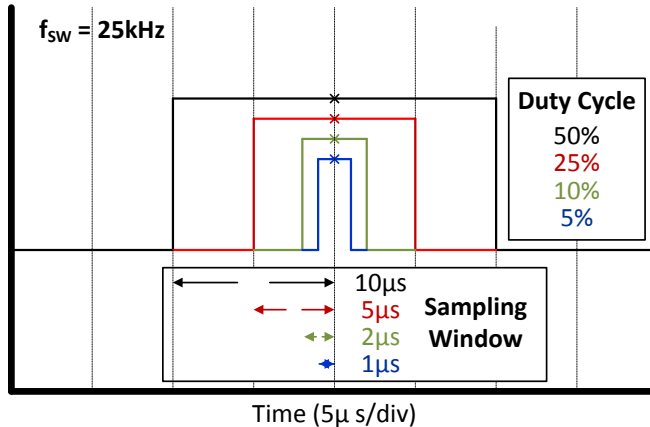


Figure 2. Duty Cycle Impact On Settling Time

An amplifier that is unable to settle within the sampling window will result in a processed waveform that is not proportional to the phase current signal reducing the effectiveness of the motor control algorithms. Figure 3 shows how the output of an amplifier that has insufficient bandwidth and output drive capability will appear. As the input current signal is switching the amplifier's output is unable to reach and settle to the proportional output voltage level resulting in a triangle wave form.

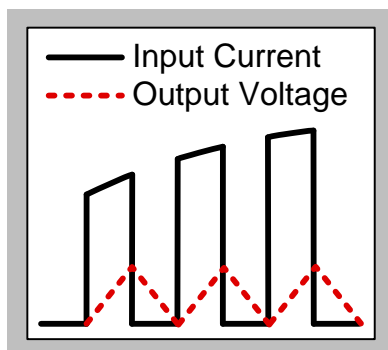


Figure 3. Slew Rate Limited Output

Two amplifier parameters that determine the effectiveness for a given settling time requirement are **slew rate** and **small signal bandwidth**. The slew rate specification indicates how quickly the amplifier's output voltage can change in response to a quickly

changing input signal. An ideal amplifier's output would match the low-side phase leg's stepped input current signal. The slew rate provides an indication of the amplifier's expected delay in response to the stepped input signal.

The amplifier's small signal bandwidth also plays a large role in how the output responds to the stepped input condition. An amplifier placed in a high gain configuration has the open-loop bandwidth divided by the corresponding closed-loop gain resulting in a smaller closed-loop small signal bandwidth. Selecting an amplifier with insufficient bandwidth increases the settling time and will result in a more damped output response.

The INA301 is a high-speed current sense amplifier that combines both a high output stage drive capability with a 4V/µs slew rate and a signal bandwidth of 550kHz at a gain of 20V/V. This combination of slew rate and high-speed signal bandwidth, in addition to the on-board over-current comparator make the INA301 ideal for low-side, phase current measurements.

#### Alternate Device Recommendations

Depending on the necessary system requirement, there may be additional devices that provide the needed performance and functionality. For applications requiring lower measurement accuracy without the additional integrated comparator for over-current detection, use the INA181. For applications requiring current measurements to be taken in-line with the motor phases, use the INA240.

Table 1. Alternate Device Recommendations

Device	Optimized Parameter	Performance Trade-Off
INA181	Package: SC70-6, SOT23-6	Reduced Bandwidth & Duty Cycle Capability
INA240	Enhanced PWM Rejection for In-Line Measurements	Package Size: TSSOP-8

Table 2. Related TI TechNotes

SBOA160	Low-Drift, Precision, In-Line Motor Current Measurements With Enhanced PWM Rejection
SBOA162	Measuring Current To Detect Out-of-Range Conditions
SBOA163	High-Side Motor Current Monitoring for Over-Current Protection
SBOA165	Precision Current Measurement On High Voltage Power Rail
SBOA190	Low-Side Current Sense Circuit Integration

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated